

ASSIGNMENT [30% weightage in the final grading]

INSTRUCTION: Submit in detail report form with all the supporting code/ simulation steup file attached


Submission deadline: April 25, 2019 at 09:00 p.m.

Submit to: subasit.ece@gmail.com


Q.1: Consider a load resistance $RL=100\Omega$ to be matched to a 50Ω line with a quarter wave transformer. Find the characteristic impedance of the matching section and plot the magnitude of the reflection coefficient versus normalized frequency, f/f_0 , where f_0 is the frequency at which the line is $\lambda/4$ long.

[N.B.: First solve theoretically. Use MATLAB for coding the plot. The frequencies have to be different for every student.]

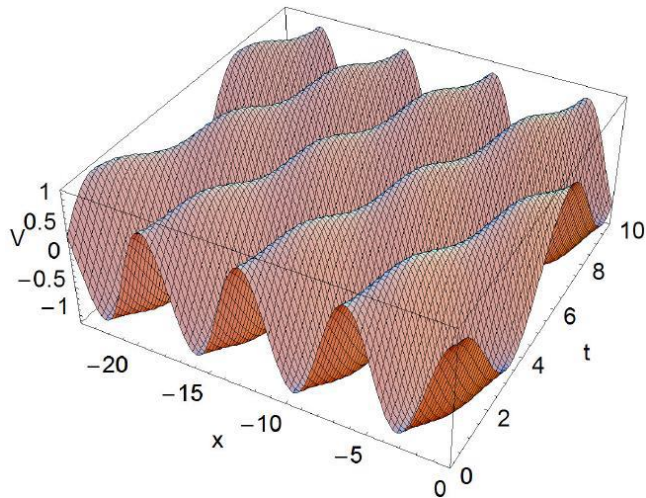Q.2: Demonstrate the following curves using MATLAB: (You are free to make suitable assumptions if needed)



Standing Wave Pattern at $\Gamma_0=0.1$

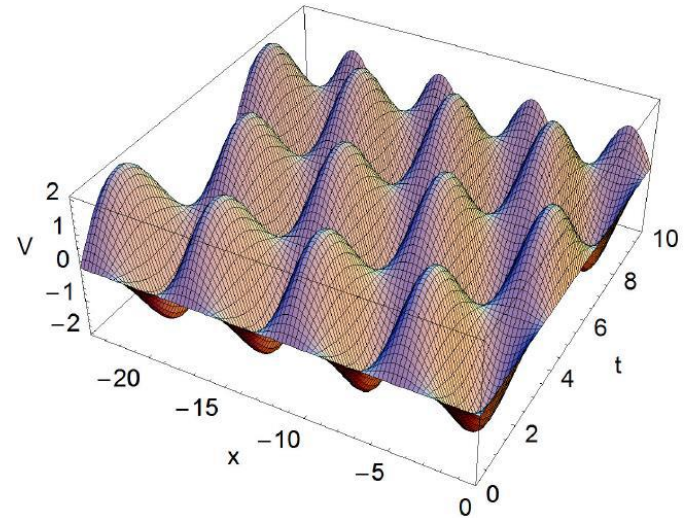


Standing Wave Pattern at $\Gamma_0=1.0$

Q.3: Write MATLAB code to determine the input impedance of a transmission line that is terminated in a **short circuit**, and whose length is:

a) $l = \lambda/8 = 0.125\lambda \Rightarrow 2\beta l = 90^\circ$

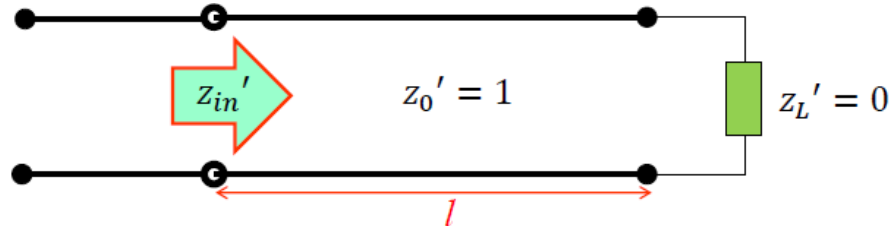b) $l = 3\lambda/8 = 0.375\lambda \Rightarrow 2\beta l = 270^\circ$



Q.4: Assignment Scope: Design a coupled-line coupler with the following specifications:

Number of sections: 5

Center Frequency: 3 GHz

Coupling: 12 dB

Port Impedance: 50Ω

Frequency Response: Maximally Flat

Assignment Tasks

- 1) Plot $|S_{11}|^2$, $|S_{21}|^2$, $|S_{31}|^2$, and $|S_{41}|^2$ in dB from 0 to 6 GHz, using a vertical scale from -50dB to 0dB. Use help of HFSS Manual to export S- matrix data, represent the matrix form in the report and then plot it using MATLAB or any other graph plotting tool.
- 2) Draw an **exact** signal flow graph of **this** (4-port) directional coupler. In other words, a signal flow graph of the form below, where c is the specific **coupling coefficient** of **this** coupler at the design frequency.

